

**SECTION - A**There are **FOUR** questions in this Section. Answer any **THREE**.

1. (a) Using mesh analysis, calculate the branch currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$  and  $I_5$  for the circuit shown in Fig. for Q. 1(a). (17)

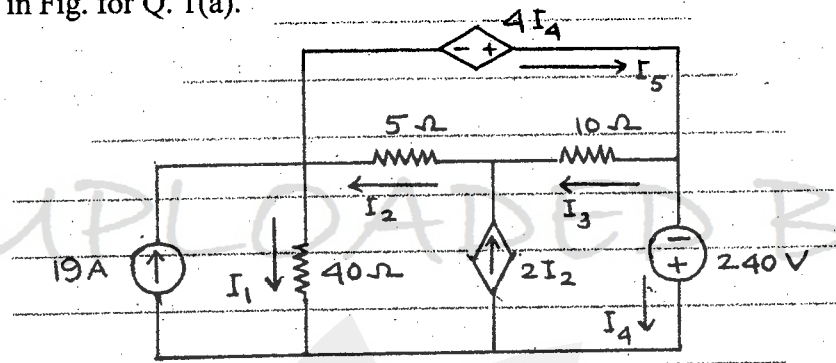


Fig. for Q. 1(a)

- (b) Find  $I_0$  using nodal analysis for the circuit shown in Fig. for Q. 1(b). (18)

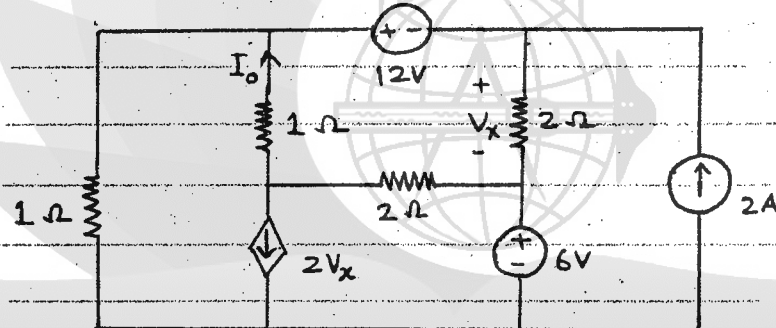


Fig. for Q. 1(b)

2. (a) Find the value of  $V_0$  using principle of superposition for the circuit shown in Fig. for Q. 2(a). (17)


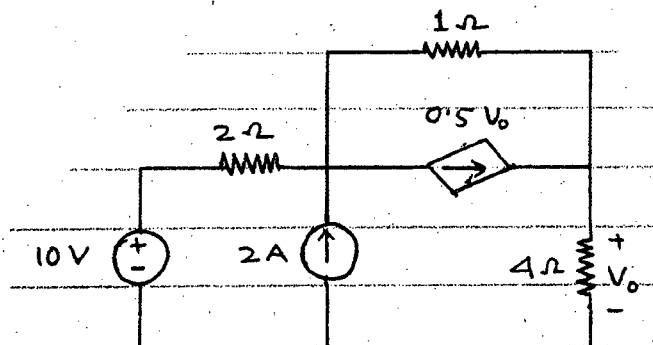


Fig. for Q. 2(a)


**EEE 101**

**Contd ... Q. No. 2**

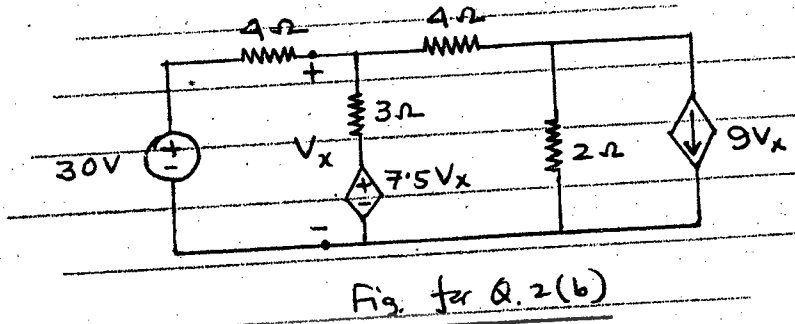
- (b) Find the value of  $V_x$  using source transformations for the circuit shown in Fig. for Q. 2(b). (18)



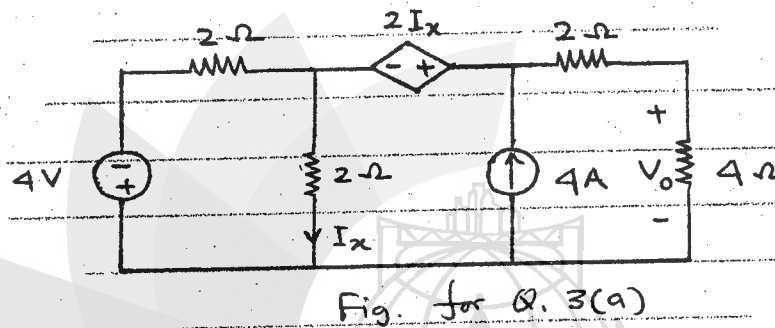3. (a) Find the value of  $V_o$  using Thevenin's theorem for the circuit shown in Fig. for Q. 3(a). (17)



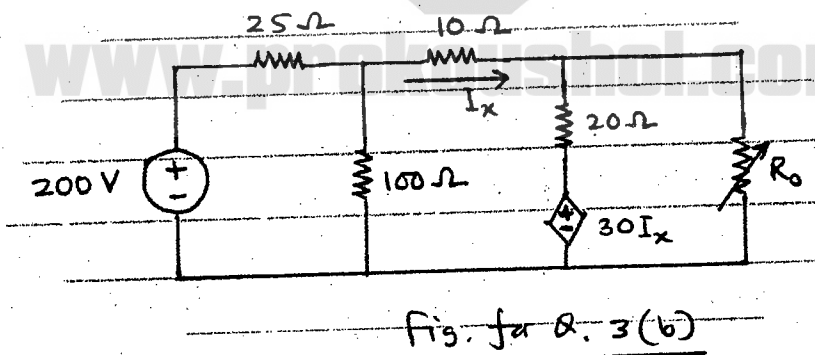- (b) The variable resistor ( $R_o$ ) in the circuit shown in Fig. for Q. 3(b) is adjusted until the power dissipated in the resistor ( $R_o$ ) is 250 W. Find the values of  $R_o$  which satisfy this condition. (18)



4. (a) Define the flux density, permeability and magnetizing force. (9)  
 (b) Explain the Ampere's Circuital Law. (6)  
 (c) Determine the value of current  $I$  required to establish a flux of  $\phi = 1.8 \times 10^{-4}$  Wb in the air gap in Fig. for Q. 4(c). (20)

**EEE 101**

**SECTION - B**

There are **FOUR** questions in this Section. Answer any **THREE**.

5. (a) Determine a numerical value for each current and voltage ( $i_1$ ,  $v_1$ , etc.) in the circuit Fig. for Q 5(a). Also calculate the power absorbed by each element and verify that the sum to zero. (20)
- (b) Calculate  $R_{ab}$  for each of the networks shown in Fig. for Q. 5(b). (15)
6. (a) For the circuit of Fig. for Q. 6(a) (15)
  - (i) Determine the output voltage  $V_{out}$  and output current  $I_{out}$ .
  - (ii) Determine the voltage gain  $|V_{out}/V_{in}|$ . (20)
- (b) Find  $R_{eq}$  and  $I$  in the circuit of Fig. for Q. 6(b).
7. (a) Obtain expressions for both  $i_1(t)$  and  $i_2(t)$  as labeled in Fig. for Q. 7(a) which are valid for  $t > 0$ . (17)
- (b) The switch in Fig. for Q. 7(b) has been closed for a long time before opening at  $t = 0$ . (18)
- Find
  - (i)  $i_L(t)$ ,  $t \geq 0$
  - (ii)  $v_L(t)$ ,  $t \geq 0^+$
  - (iii)  $v_1(t)$ ,  $t \geq 0^+$
8. (a) The current shown in Fig. for Q 8(a) is applied to a  $0.5 \mu F$  capacitor. The initial voltage on the capacitor is zero. (15)
  - (i) Find the charge on the capacitor at  $t = 15 \mu s$ .
  - (ii) How much energy is stored in the capacitor by this current?
  - (iii) Sketch  $v(t)$  over the interval  $0 \leq t \leq 50 \mu s$ .
- (b) Sketch the voltage  $v_c(t)$  as shown in Fig. for Q. 8(b) for the interval  $-0.5 \leq t \leq 40 s$ . (20)

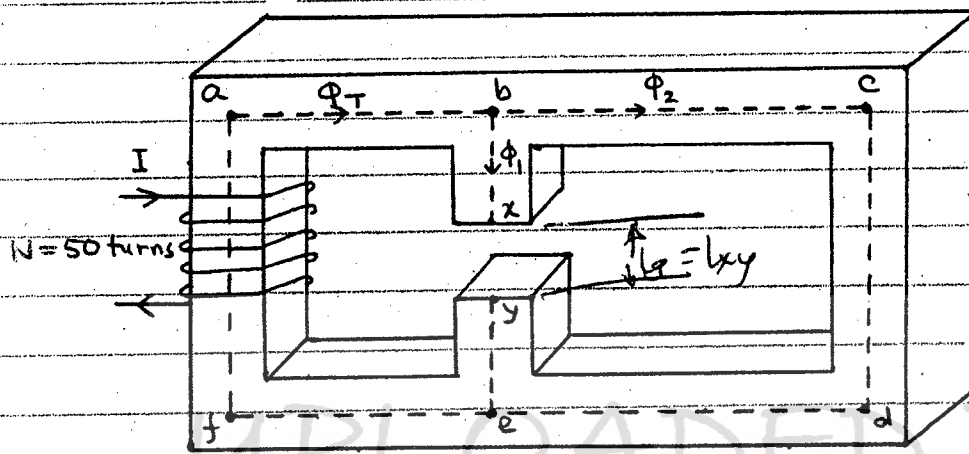


Fig. for Q. 4(c)

Given, Cross-sectional area (throughout),  $A = 6 \times 10^{-4} \text{ m}^2$

$$l_{bcde} = 0.2 \text{ m}$$

$$l_{efab} = 0.1 \text{ m}$$

$$l_{gx} = l_{gy} = 2.5 \text{ cm}$$

$$l_g = l_{ny} = 0.2 \text{ mm}$$

Material: sheet steel.

Fig. for Q. 4(c)

www.prokoushol.com

EEE 101

= 4 =

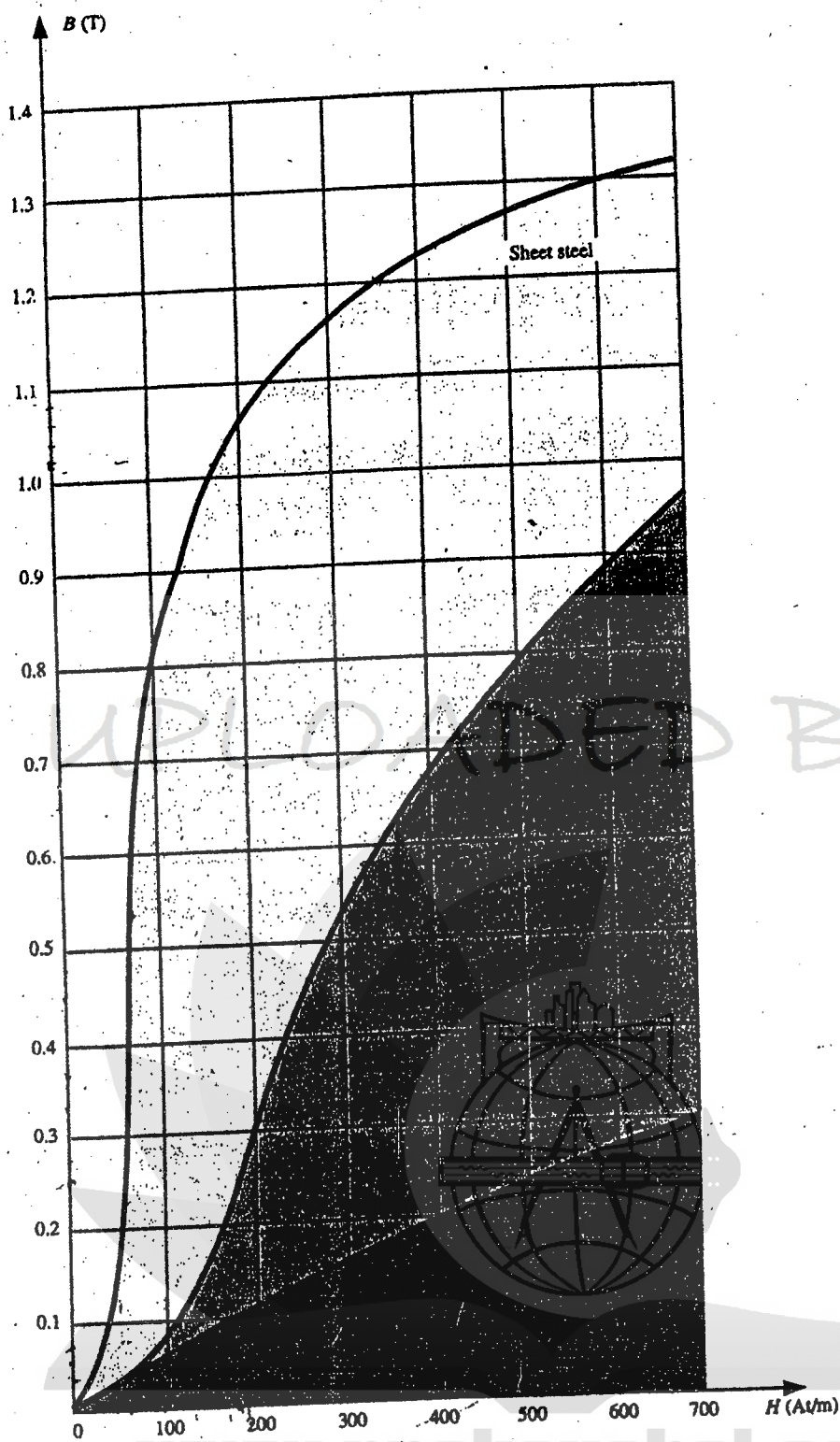


Fig. for Q. 4(c)

= 5 =



UPLOADED BY



[www.prokoushol.com](http://www.prokoushol.com)

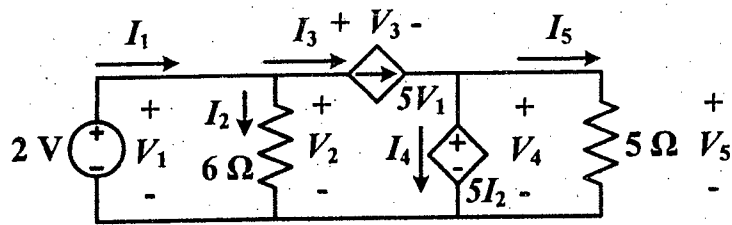


Fig. for Q. 5(a)

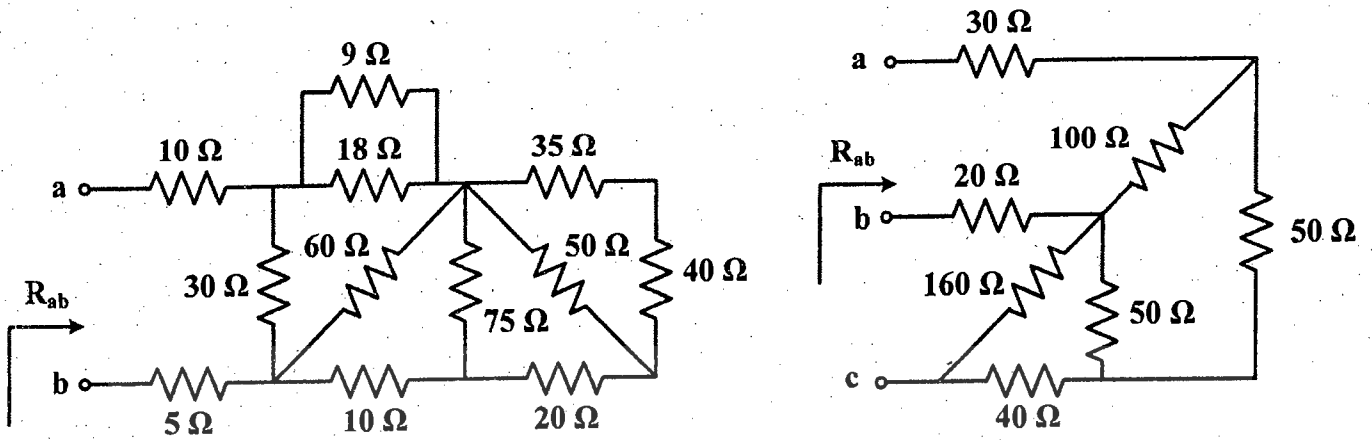


Fig. for Q. 5(b)

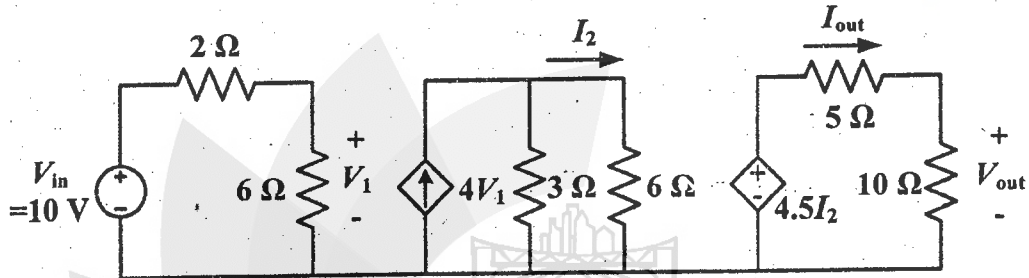


Fig. for Q. 6(a)

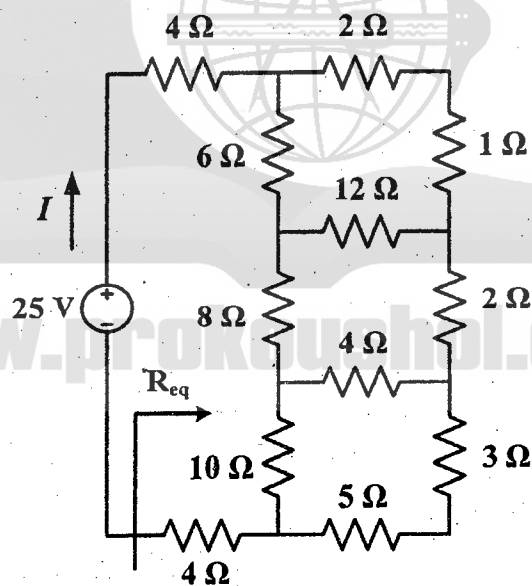


Fig. for Q. 6(b)

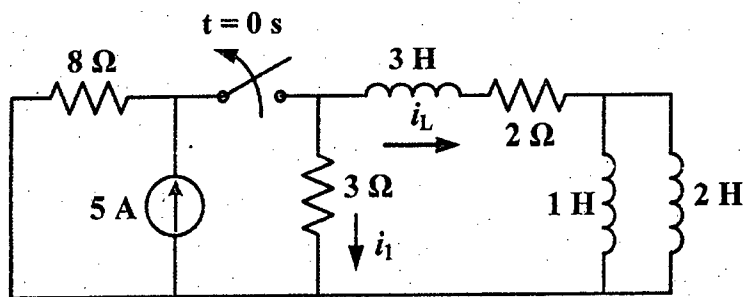


Fig. for Q. 7(a)

= 6 =

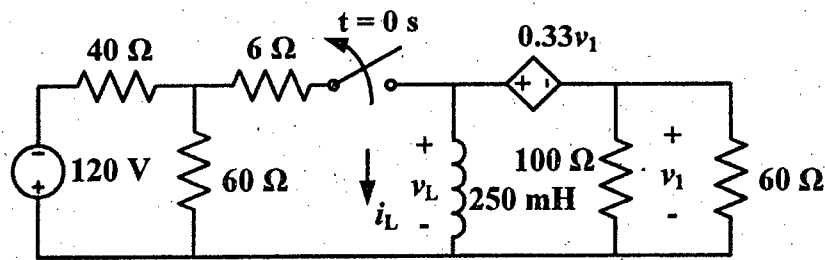


Fig. for Q. 7(b)

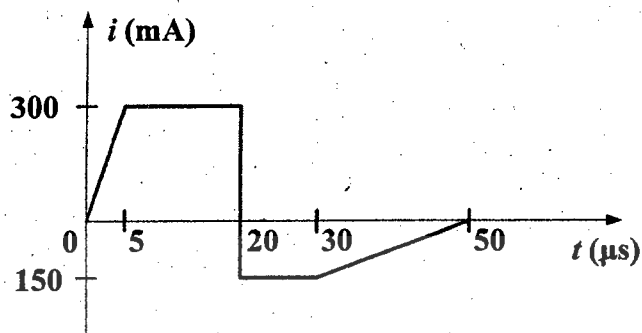


Fig. for Q. 8(a)

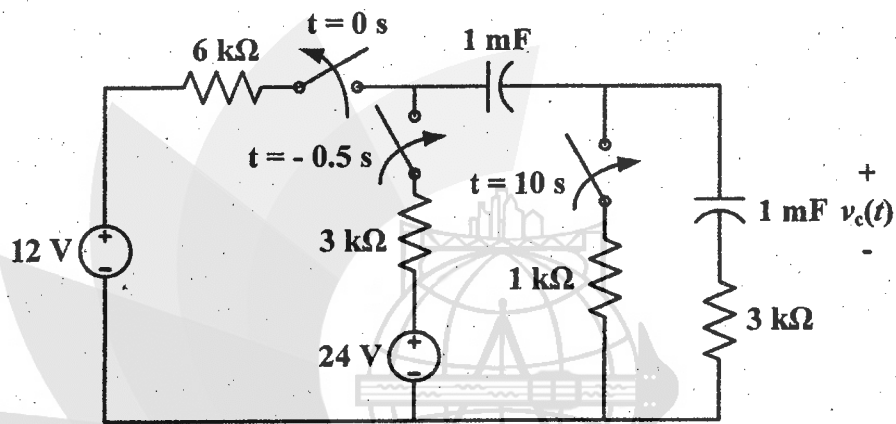


Fig. for Q. 8(b)